

**Electric Potential and Capacitance-3**


1. Two identical capacitors 1 and 2 are connected in series as shown. The capacitor 2 contains a dielectric of constant  $K$ .  $Q_1$  and  $Q_2$  are the charges stored in the capacitor. Now dielectric is removed, then  $Q_1'$  and  $Q_2'$  are the charges stored subsequently. Then

(A)  $\frac{Q_1'}{Q_1} = \frac{(K+1)}{K}$

(B)  $\frac{Q_2'}{Q_2} = \frac{(K+1)}{2}$

(C)  $\frac{Q_2'}{Q_2} = \frac{(K+1)}{2K}$

(D)  $\frac{Q_1'}{Q_1} = \frac{2}{K+1}$

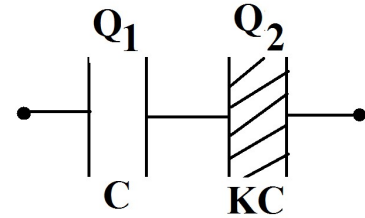

2. A capacitor is connected to a battery. The force of attraction between the plates when the separation them is halved is

- (A) remains the same                      (B) becomes twice  
 (C) becomes halved                      (D) becomes four times

3. A 900 pF capacitor connected to a 100 V battery is disconnected from the battery and connected to another 900 pF capacitor. The electrostatic energy stored by the system is

- (A) 2.25  $\mu$ J              (B) 3.25  $\mu$ J              (C) 4.5  $\mu$ J              (D) 6.25  $\mu$ J

4. Three capacitors each of capacitance 9 pF are connected in series, across a 120V supply. The total capacitance of the combination and the potential difference across each capacitor are respectively:

- (A) 3 pF, 120 V    (B) 3 pF, 40 V    (C) 27 pF, 120 V    (D) 27 pF, 40 V

5. Three capacitors of capacitances 2 pF, 3 pF and 4 pF are connected in parallel across a 100V supply. The total capacitance of combination and the charge on 3 pF capacitor are respectively :

(A)  $\frac{12}{13}$  pF,  $3 \times 10^{-10}$  C                      (B) 9 pF,  $3 \times 10^{-10}$  C

(C) 9 pF,  $2 \times 10^{-10}$  C                      (D)  $\frac{13}{12}$  pF,  $2 \times 10^{-10}$  C

6. An electrical technician requires a capacitance of 2 $\mu$ F in a circuit across a potential difference of 1 kV. A large number of 1 $\mu$ f capacitors are available to him each of which can stand a potential difference of not more than 400 V. The minimum number of capacitors to accomplish this is

- (A) 6                      (B) 12                      (C) 18                      (D) 24


7. The equivalent capacitance of the following network is

(A)  $\frac{50}{3}$  pF



(B)  $\frac{100}{3}$  pF

(C) 50 pF

(D)  $\frac{200}{3}$  nF

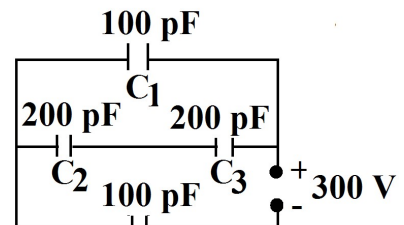

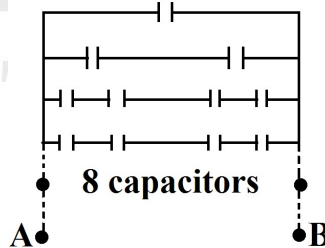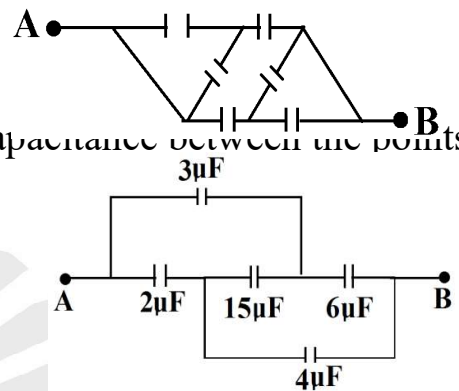8. In the above question the charge on the  $C_2$  capacitor if the network is connected to a 300V supply is  
 (A)  $10^{-8}$  C (B)  $5 \times 10^{-9}$  C (C)  $2 \times 10^{-9}$  C (D)  $2 \times 10^{-8}$  C
9. The plates of a parallel plate capacitor have an area of  $90 \text{ cm}^2$  each and are separated by 2.5 mm. The capacitor is charged by connecting it to a 400V supply. The energy per unit volume  $U =$   
 (A)  $0.075 \text{ Jm}^{-3}$  (B)  $0.113 \text{ Jm}^{-3}$  (C)  $0.256 \text{ Jm}^{-3}$  (D)  $0.475 \text{ Jm}^{-3}$
10. A  $4 \mu\text{F}$  capacitor is charged by a supply of 200 V. It is then disconnected from the supply, and is connected to another uncharged  $2 \mu\text{F}$  capacitor. The electrostatic energy of the first capacitor lost in the form of heat and electromagnetic radiation is  
 (A)  $1.25 \times 10^{-2}$  J (B)  $2.67 \times 10^{-2}$  J (C)  $1.86 \times 10^{-2}$  J (D)  $3.28 \times 10^{-2}$  J
11. Two capacitors  $C_1$  and  $C_2$  are charged to 120 V and 200 V respectively. When they are connected in parallel, it is found that potential on each one of them is zero. Therefore,  
 (A)  $5C_1 = 3C_2$  (B)  $3C_1 = 5C_2$  (C)  $3C_1 + 5C_2 = 0$  (D)  $9C_1 = 4C_2$
12. A network of six identical capacitors, each of value  $C$ , is made as shown in the figure. Equivalent capacitance between points A and B is  
 (A)  $C/4$  (B)  $3C/4$   
 (C)  $4C/3$  (D)  $3C$
13. In the circuit shown in figure, the equivalent capacitance between the points A and B is  
 (A)  $\frac{10}{3} \mu\text{F}$  (B)  $\frac{15}{14} \mu\text{F}$   
 (C)  $\frac{2}{5} \mu\text{F}$  (D)  $\frac{25}{9} \mu\text{F}$
14. A parallel plate air capacitor of capacitance  $C_0$  is connected to a cell of emf  $V$  and then disconnected from it. A dielectric slab of dielectric constant  $K$ , which can just fill the air gap of the capacitor, is now inserted in it. Which of the following is incorrect?  
 (A) The potential difference between the plates decreases  $K$  times.  
 (B) The energy stored in the capacitor decreases  $K$  times.  
 (C) The change in energy is  $\frac{1}{2} C_0 V^2 (K-1)$  (D) The change in energy is  $\frac{1}{2} C_0 V^2 \left(\frac{1}{K} - 1\right)$
15. Refer to the infinite network of capacitors shown in figure. The capacitance of each capacitor is  $1 \mu\text{F}$ . The equivalent capacity between A and B is  
 (A)  $1 \mu\text{F}$   
 (B)  $2 \mu\text{F}$   
 (C)  $0 \mu\text{F}$   
 (D)  $\infty$



Physics Worksheet-9					Electric Potential and Capacitance-3					29-01-2019				
1-C	2-D	3-A	4-B	5-B	6-C	7-D	8-A	9-B	10-B	11-B	12-C	13-A	14-D	15-B